



TOSHKENT KIMYO-TEKNOLOGIYA INSTITUTI

SHAHRISABZ FILIALI

FIZIKA

Fanidan amaliy mashg'ulot

Tokning ishi va quvvati. Joul -Lens qonuni. Kirxgoff qoidalari



Shahrisabz-2020

Bahromova Anzura



1. 19.26. Akkumulyatorlar batareyasining EYuK $\varepsilon=12\text{V}$, qisqa tutashuv- ning tok kuchi $I=5\text{A}$. Shunday batareyaga ulangan tashqi zanjirda qanday eng katta quvvat P_{max} olish mumkin?

Berilgan

$$\varepsilon=12\text{V}$$

$$I_{q.t}=5\text{A}$$

P-?

Yechilishi

$$r = \frac{\varepsilon}{I_{q.t}}$$

$$I = \frac{\varepsilon}{R+r} = \frac{\varepsilon}{2r} = \frac{\varepsilon I_{q.t}}{2\varepsilon} = \frac{I_{q.t}}{2}$$

$$P = IU = I^2 R = I^2 r = \frac{I_{q.t}^2}{4} \cdot \frac{\varepsilon}{I_{q.t}} = \frac{I_{q.t} \varepsilon}{4}$$

$$P = \frac{5 \cdot 12}{4} = 15\text{Vt}$$





2. 19.25. Ketma-ket ulangan lampochka va reostat tok manbaiga tutashtirilgan. Lampochka qisqichlaridagi kuchlanish $U=40\text{ V}$, reostatning qarshiligi $R=10\ \Omega$. Tashqi zanjir $P=120\text{ Vt}$ quvvat iste'mol qiladi. Zanjirdagi tok kuchi I topilsin.

Berilgan

$$U=40\text{ V}$$

$$R=10\ \Omega$$

$$P=120\text{ Vt}$$

I -?

Yechilishi

$$P= I^2 R_e$$

$$R_1 = \frac{U}{I}$$

$$R_e = R + R_1$$

$$P= I^2 \left(R + \frac{U}{I} \right) = I^2 R + IU$$

$$I^2 R + IU - P = 0$$

$$10 I^2 + 40I - 120 = 0$$

$$I^2 + 4I - 12 = 0$$

$$I = 2\text{ A}$$


3. 19.30. Elektr qaynatgichning o'rami ikki bo'limga ega. Agar faqat birinchi bo'lim ulansa, unda suv $t_1=15$ min da qaynaydi. Faqat ikkinchisi ulanganda esa $t_2 = 30$ min da qaynaydi. Agar ikkala bo'lim ham ketma-ket; parallel ulansa suv necha minutdan keyin qaynaydi?

Berilgan

$$t_1 = 15 \text{ min}$$

$$t_2 = 30 \text{ min}$$

$$a) t_{kk} - ?$$

$$b) t_{pp} - ?$$

Yechilishi

$$Q = \frac{U^2}{R} t$$

$$a) Q = \frac{U^2}{R_1 + R_2} t$$

$$Q = \frac{U^2}{R_1} t_1 ; Q = \frac{U^2}{R_2} t_2$$

$$\frac{U^2}{R_1} t_1 = \frac{U^2}{R_2} t_2 ; R_1 = \frac{t_1 R_2}{t_2}$$

$$Q = \frac{U^2}{\frac{t_1}{t_2} R_2 + R_2} t_{kk} = \frac{U^2}{R_2 (\frac{t_1}{t_2} + 1)} t_{kk} ; \frac{U^2}{R_2} t_2 = \frac{U^2}{R_2 (\frac{t_1}{t_2} + 1)} t_{kk}$$

$$t_{kk} = t_1 + t_2 ; t_{kk} = 15 \text{ min} + 30 \text{ min} = 45 \text{ min}$$

$$b) t_{pp} = \frac{t_1 \cdot t_2}{t_1 + t_2} = \frac{15 \cdot 30}{15 + 30} = 10 \text{ min}$$



Topshiriq



1. Akkumulyatorlar batareyasining EYuK $\varepsilon=12\text{V}$, qisqa tutashuvning tok kuchi $I= n \text{ A}$. Shunday batareyaga ulangan tashqi zanjirda qanday eng katta quvvat P_{max} olish mumkin?
2. EYuK $\varepsilon=2\text{V}$ va ichki qarshiligi $r= n \Omega$ bo'lgan akkumulyatorlar batareyasiga o'tkazgich uladilar. 1) Unda ajraladigan quvvat maksimal bo'lishi uchun lozim bo'ladigan o'tkazgichning R qarshiligi, 2) bu holda o'tkazgichda ajraladigan quvvat P aniqlansin.
3. Batareyaning EYuK $\varepsilon=20 \text{ V}$. Tashqi zanjirning qarshiligi $R=2 \Omega$, tok kuchi $I= 4\text{A}$. Batareyaning FIK topilsin. Tashqi qarshilik R ning qanday qiymatida FIK 99% ga teng bo'ladi.



Izoh: n sonining o'rniga har bir talaba o'zining jurnaldagi nomerini masalaga qo'yib ishlaydi.